

CST Part IA: Digital Design, SV 1
Zijun Joe Yan
2016-11-13

1 Ex1

	A	B	\bar{a}	$\overline{\bar{a} + b}$	\bar{b}	$\overline{a + \bar{b}}$	x
1.1.1	0	0	1	1	1	1	0
	0	1	1	0	0	1	1
	1	0	0	1	1	0	1
	1	1	0	1	0	1	0
	0	0	1	0	1	0	1
	0	1	1	0	0	1	0
	1	0	0	1	1	0	0
	1	1	0	0	0	0	1

The first circuit is called XOR.

the second circuit is called NOR.

$$1.2.1 \quad a.b.c + a.c.\bar{c} = a.b.(c + \bar{c}) = ab$$

$$1.2.2 \quad a(\bar{a} + b) = a\bar{a} + ab = 0 + ab = ab$$

$$1.2.3 \quad (a + c)(\bar{a} + b)$$

$$\bar{a}c + ab + cb$$

$$\bar{a}c + ab + (\bar{a} + a)cb$$

$\bar{a}c + ab$ (adsorbtion) btw. this is consensus

$$1.2.4 \quad (a + c)(a + d)(b + c)(b + d)$$

$$\underline{\bar{a}c + \bar{a}\bar{d}} + \underline{\bar{b}\bar{c} + \bar{b}\bar{d}}$$

$$\bar{a} + \bar{b} + \bar{c} + \bar{d}$$

$$ab + cd$$

$$1.2.x \quad x + (\bar{x}y) = (x + \bar{x})(x + y) = 1.(x + y) = x + y$$

To prove the second equation, take complement on both side. $\overline{x + (\bar{x}y)} = \overline{x + y}$


Then the LHS will be: $\bar{x}(x + \bar{y}) = \bar{x}x + \bar{x}\bar{y} = \bar{x}\bar{y}$

So proved: $\overline{x + y} = \bar{x}\bar{y}$


To prove the third one, just replace x and y with \bar{x} and \bar{y}
and take implement on the both side on the second equation.

so proved: $\bar{x} + \bar{y} = \bar{x}\bar{y}$

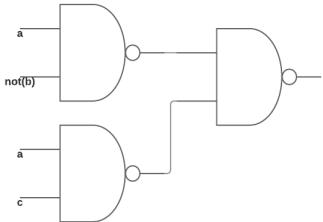
$$1.7.a \quad a\bar{b} + ac = \overline{\bar{a}\bar{b}}.\overline{ac}$$


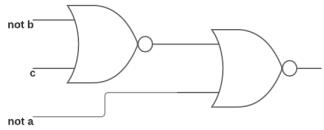
$$1.7.b \quad a(\bar{b} + c) = \overline{\bar{b} + c} + \bar{a}$$


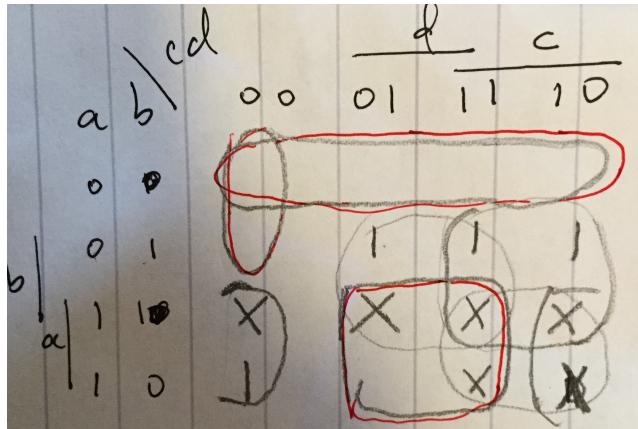
$$1.8 \quad g = 0101 + 0110 + 0111 + 1000$$



$$g = bd + bc + a\bar{d}$$

$$\bar{g} = \bar{a}\bar{b} + \bar{a}\bar{c}\bar{d} + ad$$

$$g = (a+b)(a+c+d)(\bar{a}+\bar{d})$$

$$1.11 \quad (a) 100 \ 50 \ 25 \ 12 \ 6 \ 3 \ 1$$

reverse 0010011 is 01100100

38 19 9 4 2 1

reverse 011001 is 100110

not 00100110 is 11011001

then +1 is 11011010

so 100 = 01100100₂ and -38 = 11011010₂

01100100 + 11011010 = 10011110

remove head 1 and this is 00111110 or (58)₁₀ or (3E)₁₆ which is the attempted answer.

0010 0110 0111 0101 0100 1100 1101 1111 1110 1010

actually they will go through a properly drawn 4-4 K-map in a zigzag way.

2 Ex2

I guess those are lists of binary code but no idea how to decode..

3 Ex3

(a) There are 16 possibility.

A	B	output
0	0	x
0	1	x
1	0	x
1	1	x

One truth table means one possible function. Then to fill each x with 0 or 1.

There are 2^4 possibility.

$$(b) \bar{a} = \overline{\bar{0} + a}$$

notice $\overline{\bar{a} + \bar{b}} = a.b$
so $ab = \overline{\bar{0} + a} + \overline{\bar{0} + b}$

$$(c) \bar{a} = (0 \equiv a) = (1 \oplus a)$$

$$a + b = (ab) \oplus (a \oplus b)$$

4 Ex4

$$(a) \overline{abc\dots} = \bar{a} + \bar{b} + \bar{c}\dots$$

$$a + b + c\dots = \bar{a}\bar{b}\bar{c}\dots$$

(b) Minterms: the junction of all variables in complemented or uncomplemented form
Essential terms: covers a term that no other term covers it. (Do you mean Essential Prime terms or not?)

prime terms: cannot be further combined.


(c) sum of products form: disjunctions of junction (OR of AND variables).

minimised sum of products form: simplified SOP by K-map or Q-M method

disjunctive normal form: the disjunction of its minterms

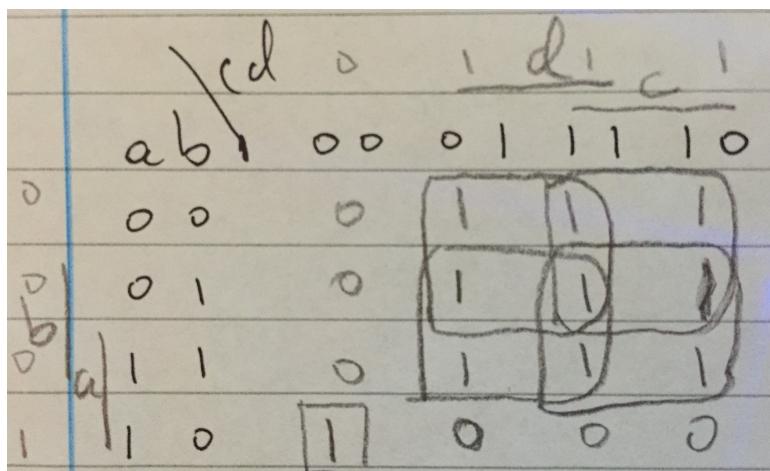(d) All circles are essential prime term.

minimum SOP: $bd + bc + \bar{a}d + \bar{a}c + \bar{a}\bar{b}\bar{c}\bar{d}$



$$(e) \bar{a}d + \bar{a}c + a\bar{c}\bar{d}$$

$$(f) f = \bar{a}\bar{c}\bar{d} + b\bar{c}\bar{d} + a\bar{b}d + a\bar{c}d$$

$$\text{minimum POS: } f = (a + c + d)(\bar{b} + c + d)(\bar{a} + b + \bar{d})(\bar{a} + c + \bar{d})$$

5 Ex5

$$(a) (X + Y)(X + Z)$$

$$\overline{X}\bar{Y} + \bar{X}\bar{Z}$$

$$\overline{X}(\bar{Z} + \bar{Y})$$

$$X + YZ$$

(b) The same as 1.2.3

(c) Tristate Buffer

$$(d) (A + B + \bar{C}DE)(A + \bar{D} + E)(\bar{A} + C)$$

$$(AC + \bar{A}(B + \bar{C}DE))(A + \bar{D} + E)$$

$$(AC + \bar{A}B + \bar{A}\bar{C}DE)(A + \bar{D} + E)$$

$$AC + AC\bar{D} + ACE + 0 + \bar{A}\bar{D}B + \bar{A}BE + 0 + 0 + \bar{A}\bar{C}DE$$

$$AC + \bar{A}\bar{D}B + \bar{A}BE + \bar{A}\bar{C}DE$$

(e) cell adjacency: 010 011 001 000 100 101 111 110

method: $a(n-1)$ and reversed $a(n-1)$ then add 0 or 1 to head.

			<u>de</u>	<u>00</u>	<u>01</u>	<u>11</u>	<u>b</u>
a	b	c	0 1 0	1	1	1	0
b	c		0 1 1	1	1	1	0
c			0 0 1	0	0	0	0
			0 0 0	0	0	1	0
			1 0 0	0	0	0	0
		c	1 0 1	1	1	1	1
b			1 1 1	1	1	1	1
			1 1 0	0	0	0	0


(f)

6 Ex6


<i>a</i>	<i>b</i>	<i>c_{in}</i>	<i>s</i>	<i>c_{out}</i>
0	0	0	0	0
0	1	0	1	0
1	0	0	1	1
1	1	0	0	0
0	0	1	1	1
0	1	1	0	0
1	0	1	0	1
1	1	1	1	1

$$s = a \oplus b \oplus c_{in}$$

$$c_{out} = a \bar{b} \oplus c_{in}$$

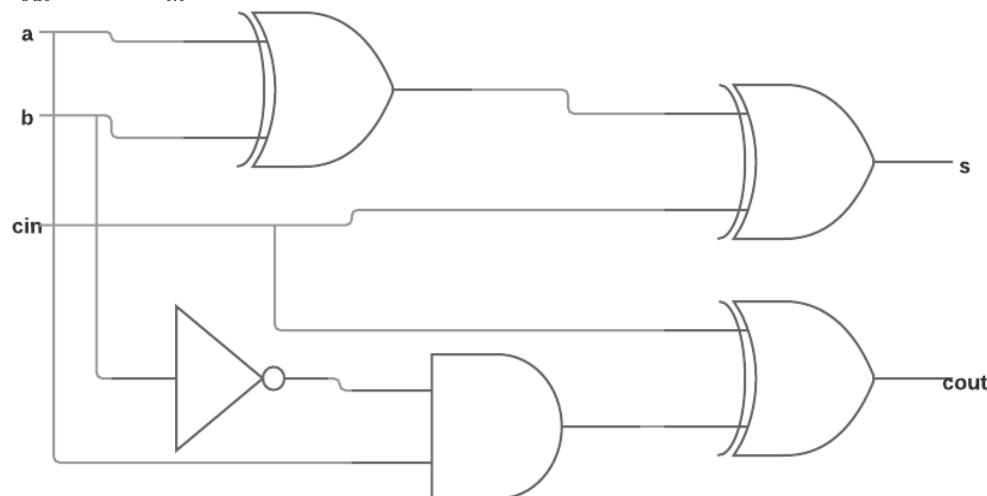

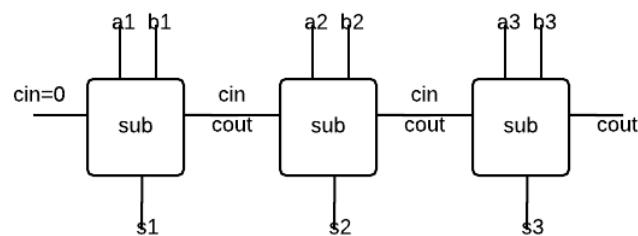The circuit above have input *a* *b* *cin* and output *s* and *cout*.
cin: 1 means need to subtract 1 0 means not.
cout: 1 means need to borrow 1 from higher digital 0 means not.



7 Ex7



- (b) The 0 0 means clear so once the first input is 0 0 then the output H should also be clear. For C, once b is logical 0 then it must be 0 (no need for add 1 to next digit) otherwise it is also clear 0 0.

A1	A0	B1	B0	H1	H0	C1	C0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0
0	1	0	0	0	0	1	0
0	1	0	1	0	1	0	1
0	1	1	0	1	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	1	0	0	1
1	0	1	0	0	1	0	0

$$\begin{array}{r}
 \begin{array}{c} B_1 B_0 \\ \hline A_1 & A_0 & 0 & 0 & 0 & 1 & 1 & 1 & 0 \end{array} \\
 \begin{array}{c} B_0 H_1 \\ \hline B_1 \end{array}
 \end{array}$$

0	0	0	0	X	0		
A ₀	0	1	0	0	X	1	
A ₁	1	0	X	X	X	X	
	1	0	0	1	X	0	

$$H_1 = A_1 B_0 + A_0 B_1$$

$$\begin{array}{r}
 \begin{array}{c} B_1 B_0 \\ \hline A_1 & A_0 & 0 & 0 & 0 & 1 & 1 & 1 & 0 \end{array} \\
 \begin{array}{c} B_0 H_1 \\ \hline B_1 \end{array}
 \end{array}$$

0	0		X				
A ₀	0	1		1	X		
A ₁	1	0	X	X	X	X	
	1	0	0	1	X	1	


$$H_0 = A_0 B_0 + A_1 B_1$$

B_0	B_1	C_1
A_1	A_0	C_1
0	0	X
A_0	0 1	X
A_1	1 0 X X X X	X X
1	0	1

$$C_1 = A_1 B_1$$

B_0	B_1	C_0	C_1
A_1	A_0	C_0	C_1
0	0	1 X	0
A_0	0 1	1 X 1	
A_1	1 0 X X X X	X X 1	X
1	0	1 X 1	

$$C_0 = A_0 + B_0$$

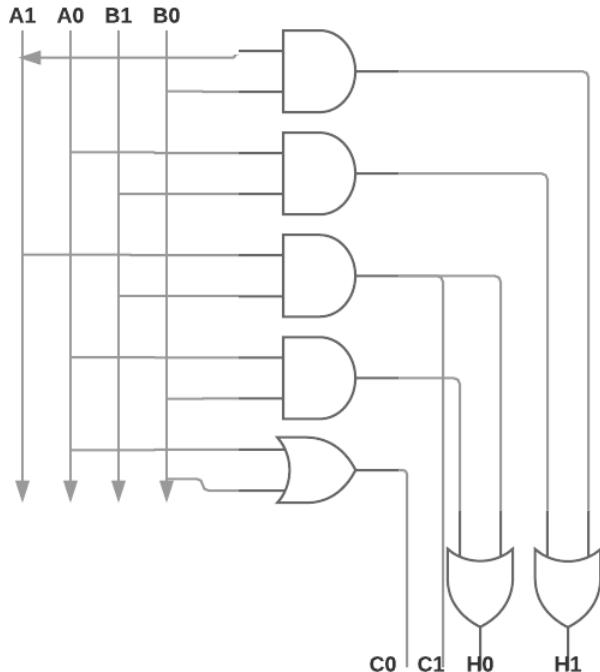

(c) This needs 7 gates. Original circuit needs 3 gates.

(d) They both have $2T$ (ps) delay.

8 Ex8

(a) $\bar{U} = U\bar{X} + \bar{U}\bar{W}\bar{Y} + \bar{U}\bar{W}\bar{Z} + \bar{U}\bar{Z}Y + X\bar{W}\bar{U}$

(b) This is exactly the same as Ex5(e).

As change A to U, B to W, C to X, D to Y, E to Z.
so $P = UX + \bar{U}\bar{Y}W + \bar{U}WZ + \bar{U}\bar{X}YZ$

(c) picture

